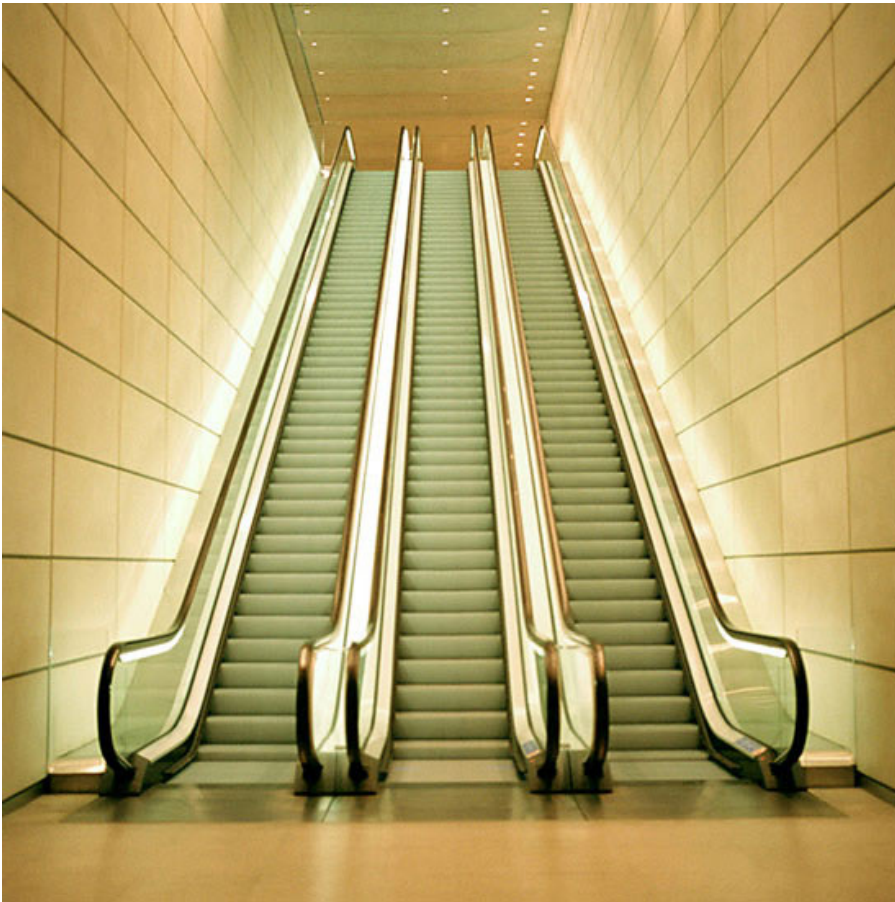


# Electrical Circuits


Let the electrons flow!
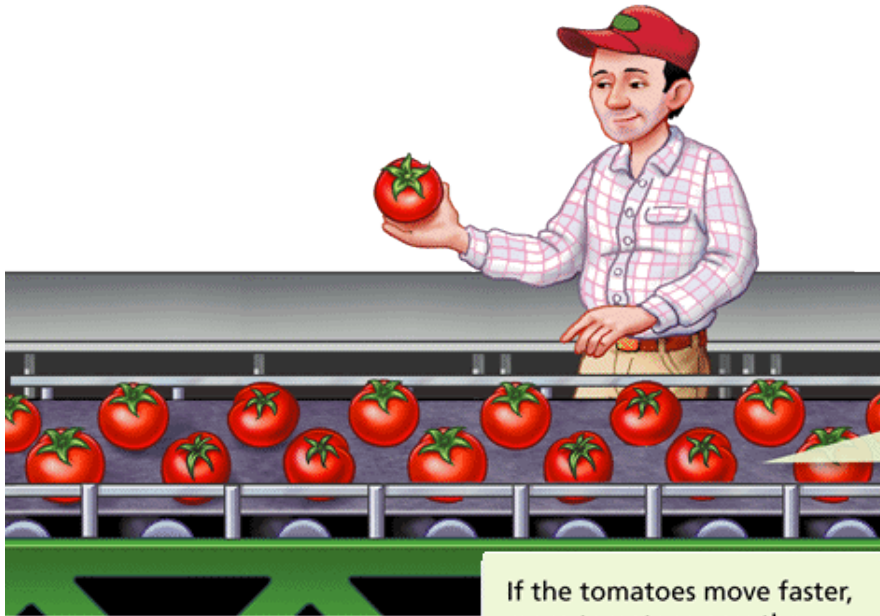
# What is an electrical current?




When you ride on an escalator you are in need of getting from one point to another, in a quick and easy way. The electric current in a wire operates on the same principal.

Current is measured as the rate, or amount, of charge that passes a specific point through a wire in a unit of time.



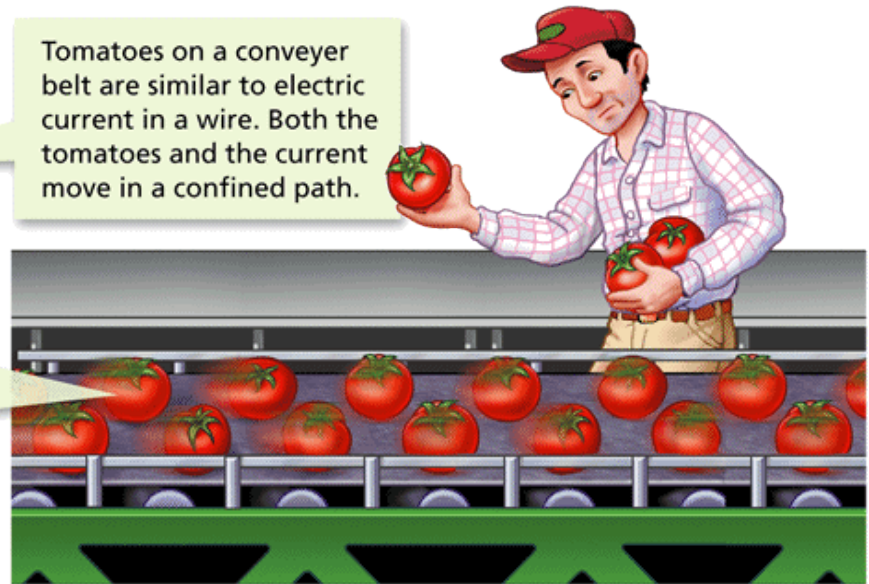If the tomatoes move faster, more tomatoes pass the worker every second. Similarly, if current is increased in a wire, more charges pass by a point on the wire every second.



Tomatoes on a conveyer belt are similar to electric current in a wire. Both the tomatoes and the current move in a confined path.


In a previous lab, you learned that the build up of electric charges on an object is called **static electricity**. Static electricity does not flow in a continuous path and that's how it differs from electric current.




*Static*

**ELECTRICITY**

*ROCKS!!!*

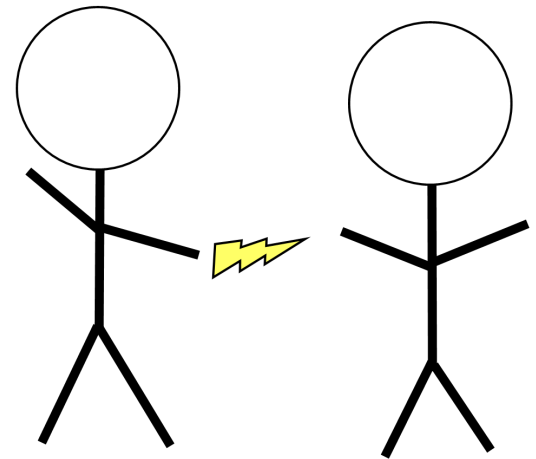


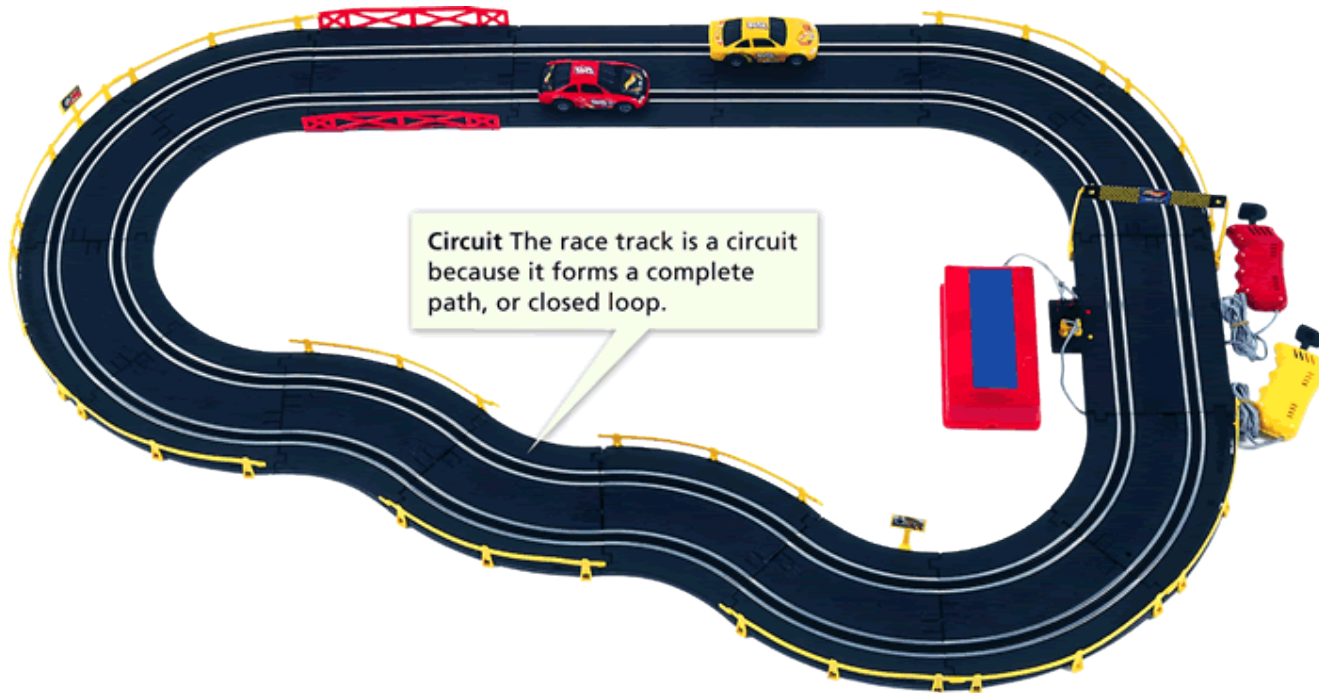An **electric circuit** is a complete, unbroken, path through which electric charges can flow.





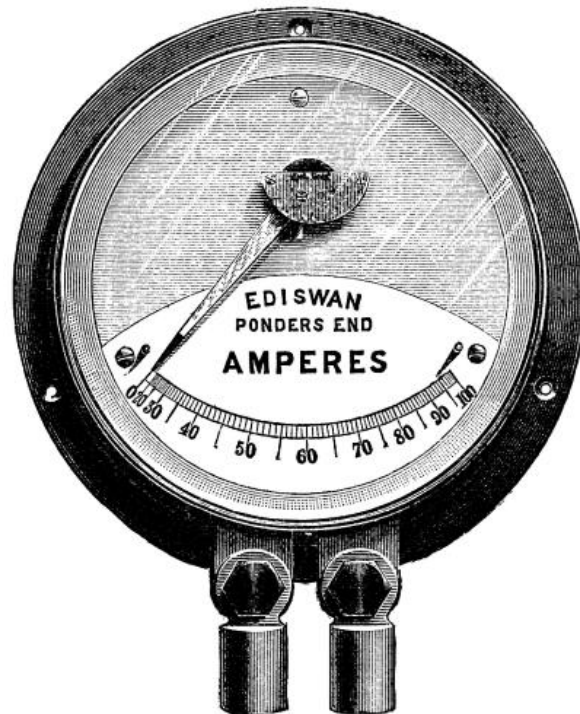The unit of measure is called the **ampere**, or **amp**, and is symbolized as **A**. Therefore, the number of amps is the amount of charge flowing passed a given point per second.




# Parts of a circuit

**Energy Source** A battery is the energy source that makes charges move around the circuit.

**Resistor** A light bulb is a resistor that transforms electrical energy to light.

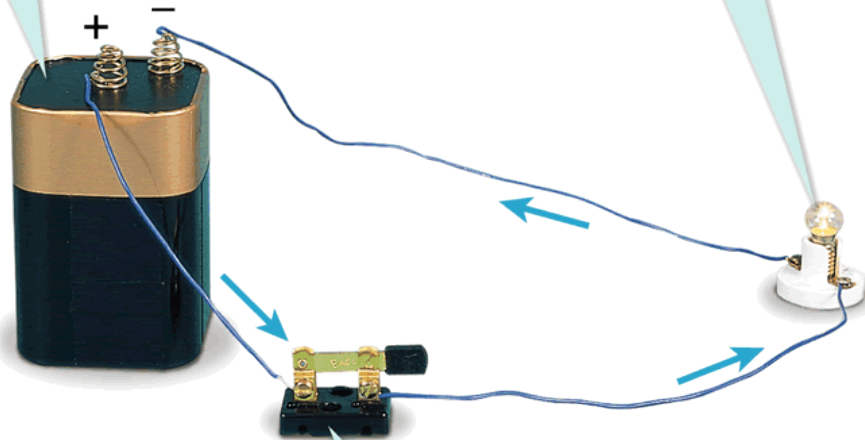
**Switch** A switch is used to open and close the circuit.



## Circuit Symbols

- Wire
- — Switch
- + — Energy source
- ⊞ Resistor

## Circuit Diagram

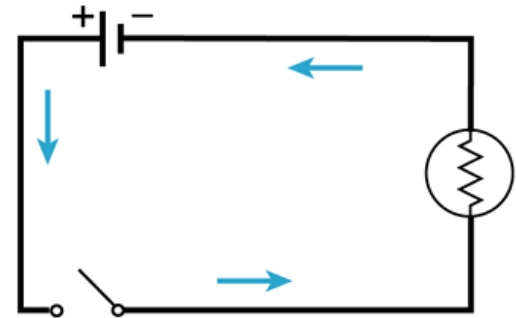

**Resistance** is the measure, in **Ohms**, of how difficult it is for a charge to flow through a material. The greater the resistance the less current.





**Resistance:** . There are four factors which determine a material's resistance:

- 1. What the material is made from.** Insulators have high resistance while conductors have low resistance.
- 2. The length of the material.** Long wires have more resistance than short wires. (Example- water flowing out of a long pipe versus a short pipe)
- 3. Diameter (gauge) of the material.** Thin wires have more resistance than thick wires. (Example-small diameter pipe has less water flowing out of it than large diameter pipe)
- 4. Temperature of the material.** Resistance increases as temperature increases.

# Think about this!

